

Digital Logic Design

Hajar Falahati



Department of Computer Engineering
IRAN University of Science and Technology

hfalahati@iust.ac.ir



Hazard

- **Static Hazard**

  - Two-level SOP (AND-OR) circuit
 - It may have static-1 hazards
- Two-level POS (OR-AND) circuit
 - It may have static-0 hazards





- **Dynamic Hazard**

  

- **Hazard-free realization**

  - Use the **complete sum or complete product**.
- Do not cover don't cares.



Outline

- Hierarchical Design
- Combinational Logic
- Famous Combinational Logic




Implementation

- Digital circuit **design**:
 - Specification
 - Formulation and truth table
 - Optimization
 - Word description of a function
 - ⇒ a set of switching equations
 - Hardware realization
 - Technology Mapping
- Gate-level design
 - Connect Logic gates




Complex Design

- How about **complex design**?

 

Intel Kaby Lake

  CORE i7 inside	 CORE i5 inside	 CORE i3 inside	 CORE i7 inside	 CORE i7 inside
Y-SERIES	U-SERIES	H-SERIES	S-SERIES	
2 in 1 Detachables, Tablets and Compute Stick	Thin Light Notebooks, Portable AIO, Minis and Conference Room	Ultimate Mobile Performance, Mobile Workstations	Desktop Performance to Value, AIO and Minis	



- 64- bit processor
- 4 cores, 8 threads
- 1.75B transistor
- 14 nm

Hierarchical Design


Logic Components

- Logic component or blocks

- Constructed via logic gates
- A set of m boolean inputs
- A set of n boolean outputs
- n switching functions
 - Each mapping the 2^m input combinations to an output
 - Current output depends only on the current input values


- Types

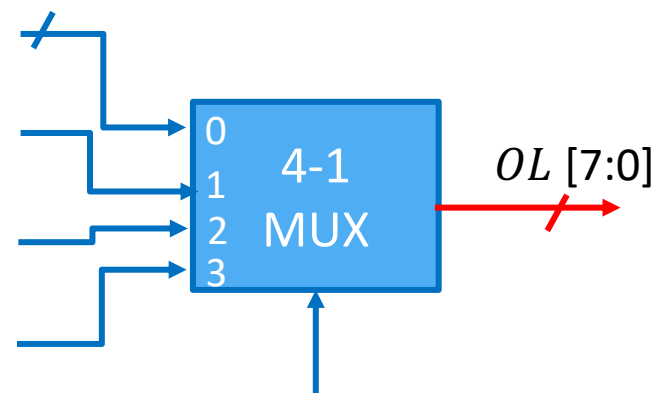- Combinational
 - Does **not have memory**
- Sequential
 - Has memory



Component-Level Design

 - Connect logic components
- Control complexity of function




Hierarchical Design

- **Step 1.** Decompose the function into smaller pieces, a.k.a., *blocks*
- **Step2:** Decompose each block's function into smaller blocks
- Repeat step2 until all resulted blocks are small enough
- **Primitive Block**
 - A block that can not be decomposed

Top-Down


- To gain **insights** into **its compositional sub-systems**
 - Reverse engineering fashion
- **Extensive planning and research phase**
 - -> Leads to development of a product
- **Structural control of a project**
- **More straightforward**

Top Down


 


Buttom-Up

 
- Piecing together of systems to give rise to more complex systems
- More **optimized**
- More **realistic**



ALU

  


ALU...

 

Combinational Logics

Combinational Logics

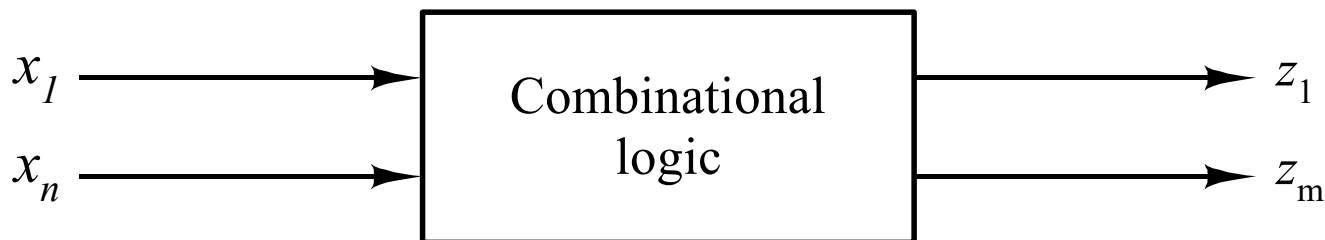
- **Always Current inputs** produce the **output**
- **Output is independent of**
 - **Sequence of inputs**
 - **Time of applying inputs**
- => **Combinational logics** are memory less
 - **Memory-less circuits** **do not** contain any **feedback** lines



Decoder


Decoder

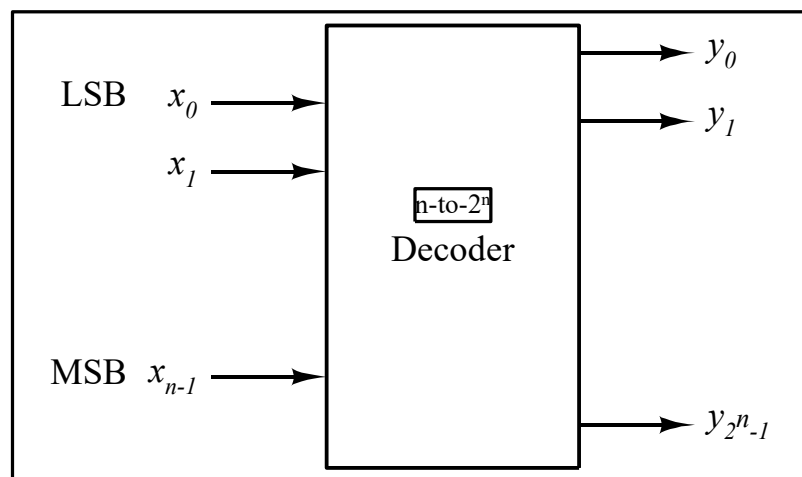- n inputs and 2^n outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- Function
 - Decoding
 - Each valid code word produces a unique output code



Decoder Implementation

- The **one output** that is **logically 1** is the output corresponding to the **input pattern** that the **logic circuit is expected to detect**
- Generate 2^n (or fewer) minterms for the n input variables

 

Decoder 1-2

- Input

- 1 bit

- Output

- 2 bit



Decoder 1-2

- **Input**


- 1 bit

- **Output**

- 2 bit




I_0	Y_0	Y_1
0	1	0
1	0	1

 

Decoder 2-4

- Input
 - 2 bit
- Output
 - 4-bit

 


Decoder 2-4

- **Input**

- 2 bit

- **Output**

- 4-bit

 

I_1	I_0	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Decoder 2-4



- **Input**

- 2 bit

- **Output**

- 4-bit

I_1	I_0	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

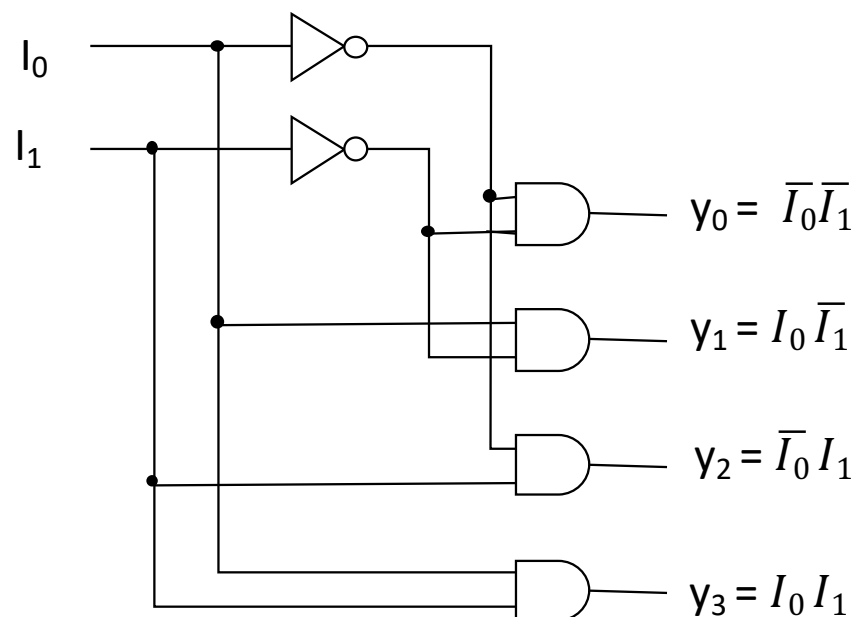 


Decoder with Enable


- **Input:** n-bit code and 1-bit enable (EN)
- **Output:** m-bit; $n \leq m \leq 2^n$
- **Function**
 - If EN=0 do **nothing**
 - If EN=1 **decoding**

Decoder with Enable: 2-4

 - **Input:** n-bit code and 1-bit enable (EN)
- **Output:** m-bit; $n \leq m \leq 2^n$
- **Function**
 - If EN=0 do **nothing**
 - If EN=1 **decoding**




Decoder with Enable: 2-4 (cont'd)

 


EN	A₁	A₀	D₀	D₁	D₂	D₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1


Decoder with Enable: 2-4 (cont'd)

 

EN	A_1	A_0	D_0	D_1	D_2	D_3
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 


Decoder 2-4: Active Low

 


S1	S0	D0	D1	D2	D3
L	L	L	H	H	H
L	H	H	L	H	H
H	L	H	H	L	H
H	H	H	H	H	L

Decoder 2-4: Active Low (cont'd)

 


S1	S0	D0	D1	D2	D3
L	L	L	H	H	H
L	H	H	L	H	H
H	L	H	H	L	H
H	H	H	H	H	L

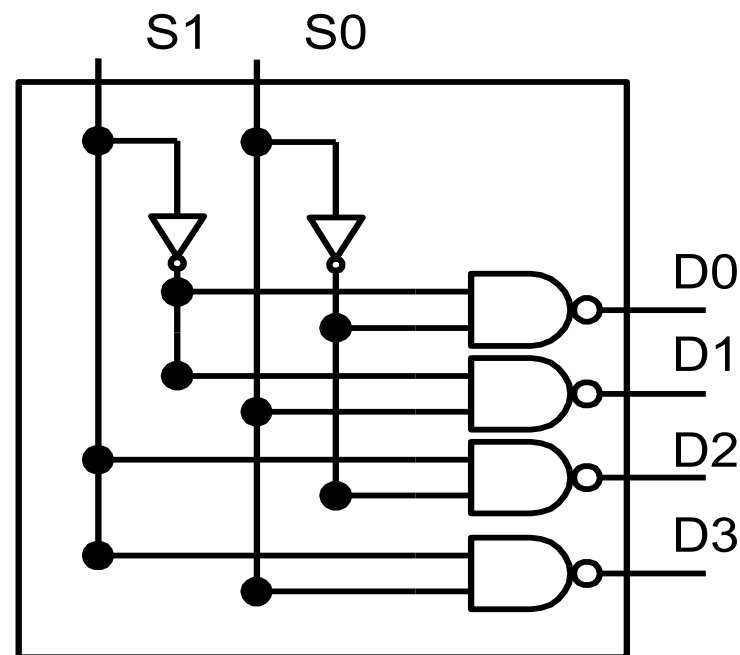

Decoder with enable:2-4: Active Low

- Output
 - Maxterms

 

(a) Logic diagram

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0


(b) Truth table

How About Larger Decoders?


- 3-8 Decoder
- 4-16 Decoder
- 5-32 Decoder
- 10-1024 Decoder
- 11-2048 Decoder

Decoder 1-2 and 2-4

I_0	Y_0	Y_1
0	1	0
1	0	1

 

I_1	I_0	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

Decoder 2-4 is made up of 2 decoder 1-2 and 4 AND gates

Expansion

- Combine two or more small circuits to form a larger one
 - Using enable signal
- Decoder expansion
 - E.g., construct decoder 3-8 from decoder 2-4

Decoder 3-8

- Design a 3-8 decoder using 2-4 decoder?

Decoder 3-8: Truth Table

S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

S_2	S_1	S_0	Y_0	Y_1	Y_2	Y_3	Y_4	Y_5	Y_6	Y_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Expansion: Decoder 3-8

• Decoder 3-8


- Two 2-4 decoder
- MSB is connected to the enable inputs
- if $S_2=0$, upper is enabled
- if $S_2=1$, lower is enabled.

S_1	S_0	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

S_2	S_1	S_0	Y_0	Y_1	Y_2	Y_3	Y_4	Y_5	Y_6	Y_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Expansion: Decoder 3-8 (cont'd)


S_2	S_1	S_0	Y_0	Y_1	Y_2	Y_3	Y_4	Y_5	Y_6	Y_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

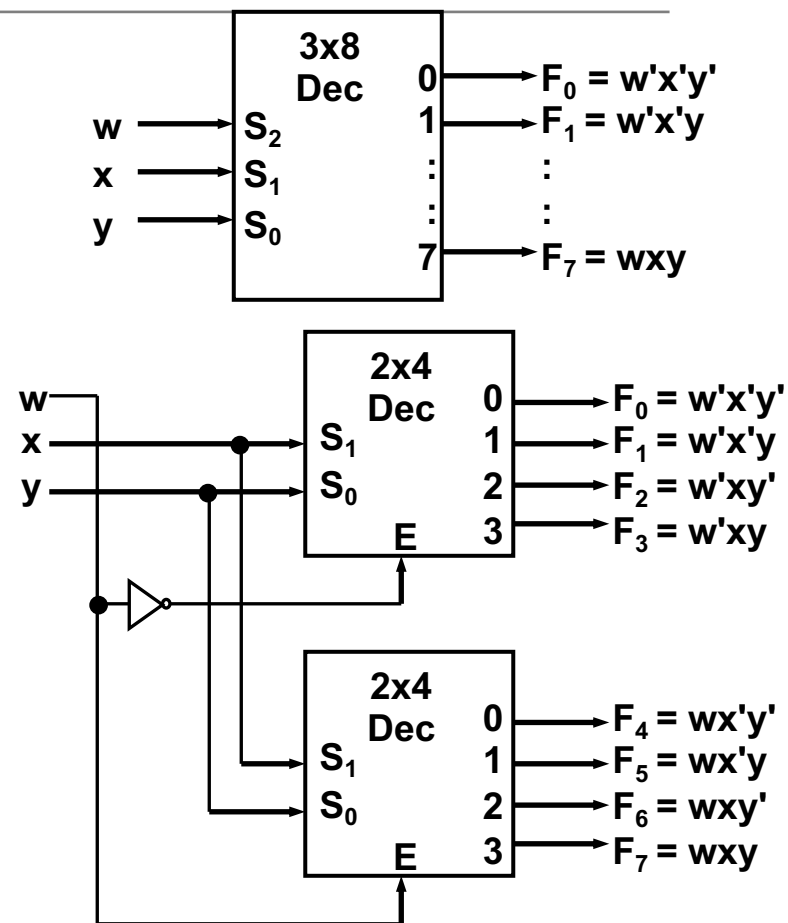

Decoder 3-8: Logic Diagram


- Input: 3-bit code and 1-bit enable (EN)
- Output: 8-bit

A2	A1	A0	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

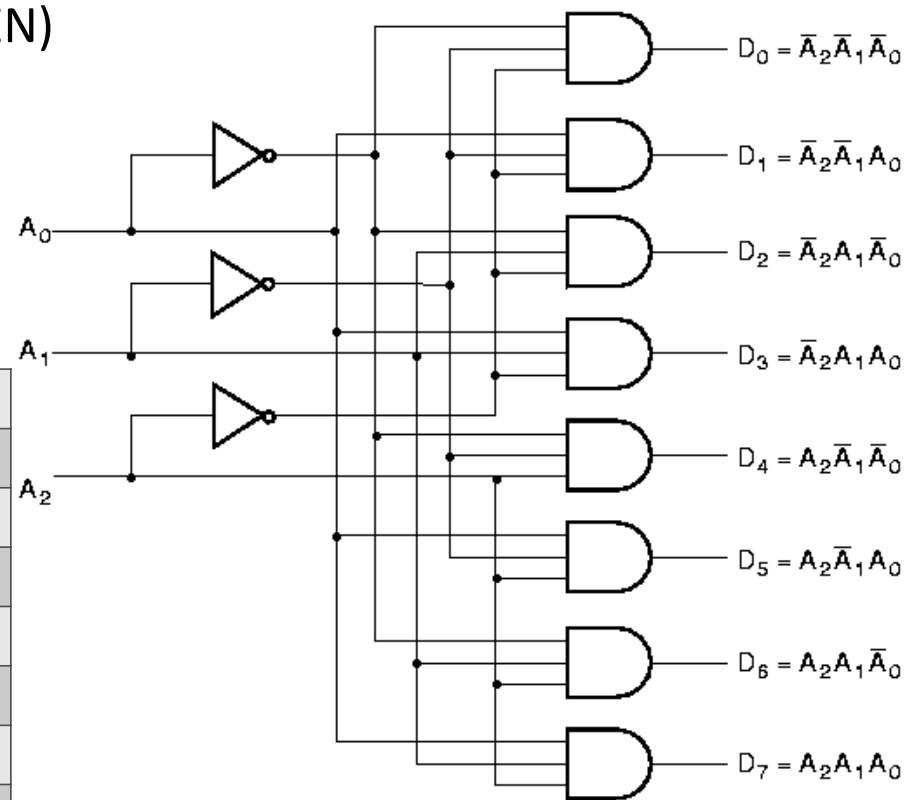



Decoder 4-16 using Decoder 3-8

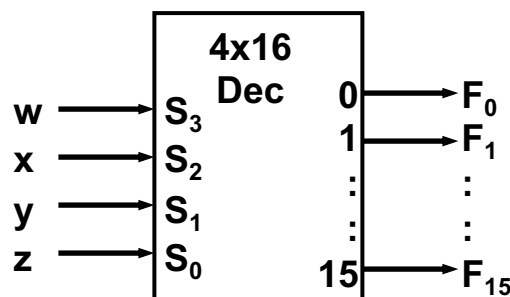- Implement 4-16 decoder
 - Using 3-8 decoders





Check
Yourself 😊

Decoder 4-16 using Decoder 3-8 (cont'd)

  


Decoder 4-16 using Decoder 2-4

  - Implement 4-16 decoder
 - Using 2-4 decoders



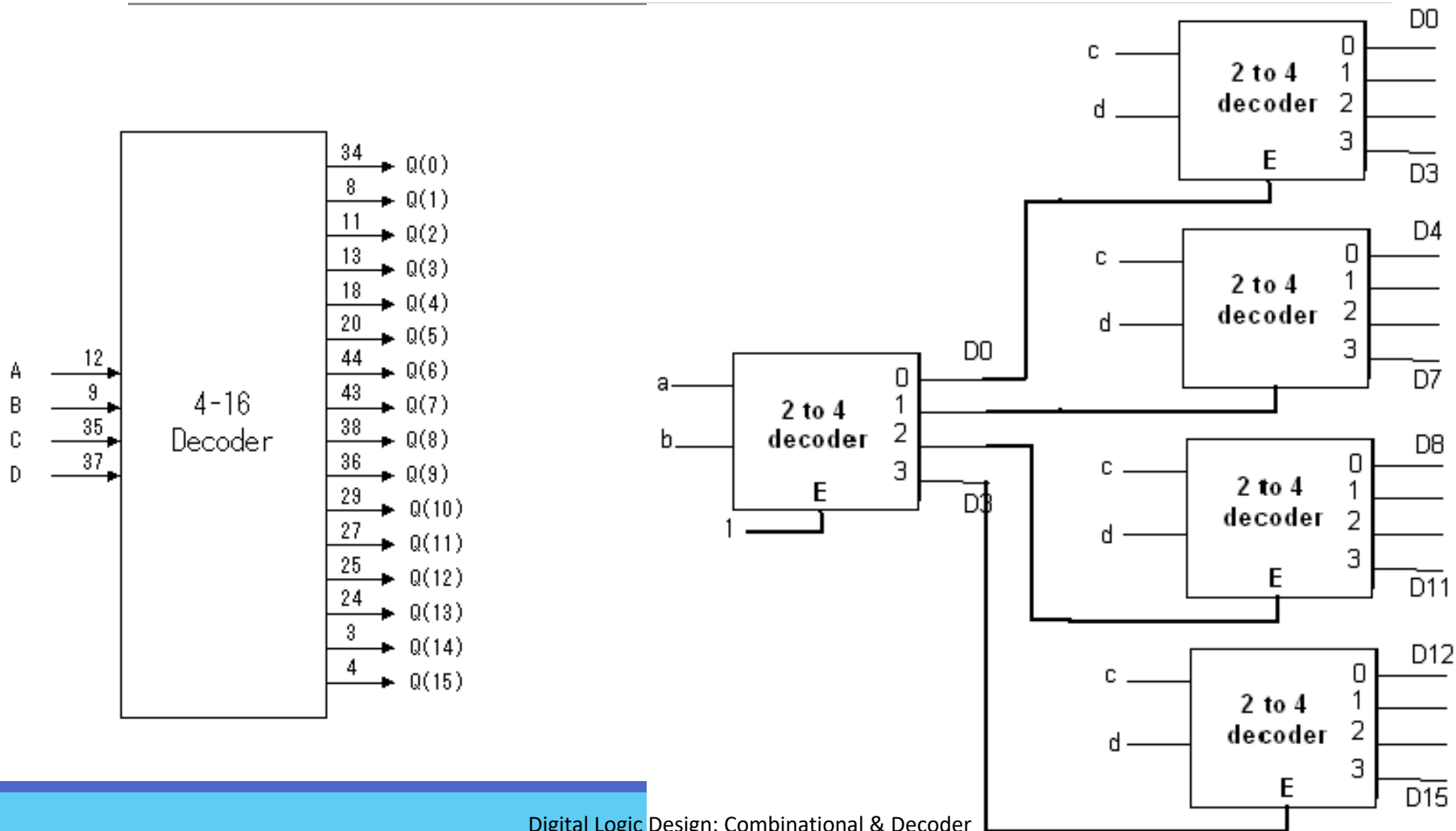Expansion: Decoder 4-16: Sample2 (cont'd)



Implementation Using Decoder

Decoder as a Logic Block

- Implement function f using decoder
 - $f(Q,X,P) = \sum m(0,1,4,6,7)$

Truth Table



- Truth table for $f(Q,X,P) = \sum m(0,1,4,6,7)$
- Consider the truth table of a 3-8 decoder

Q	X	P	y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Q	X	P	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Realization

- $f(Q, X, P) = \sum m(0, 1, 4, 6, 7)$

 
 


Sample 1

- Implement function f using decoder
 - $f(Q,X,P) = \prod M(2,3,5)$

Sample1: Realization

- Implement function f using decoder
 - $f(Q, X, P) = \prod M(2, 3, 5)$

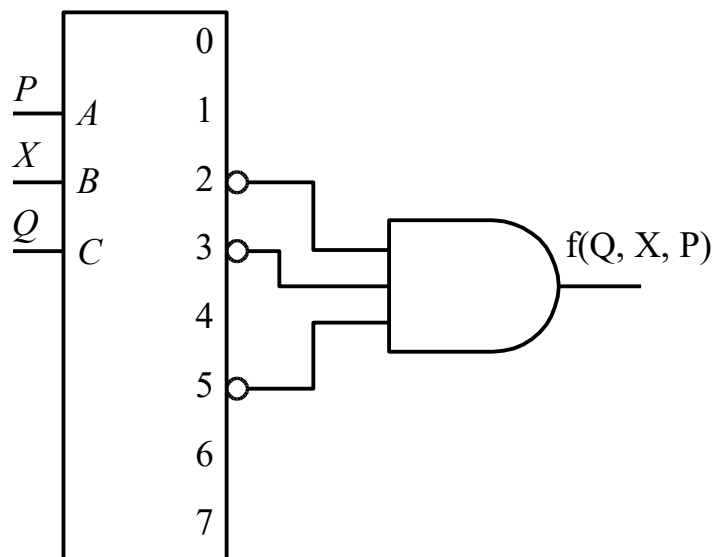 

Sample 2

- Implement a full adder using decoder

Full Adder: Truth Table

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S(x, y, z) = \sum m(1, 2, 4, 7)$$

$$C(x, y, z) = \sum m(3, 5, 6, 7)$$

Full Adder: Realization

$$S(x, y, z) = \sum m(1, 2, 4, 7)$$


$$C(x, y, z) = \sum m(3, 5, 6, 7)$$

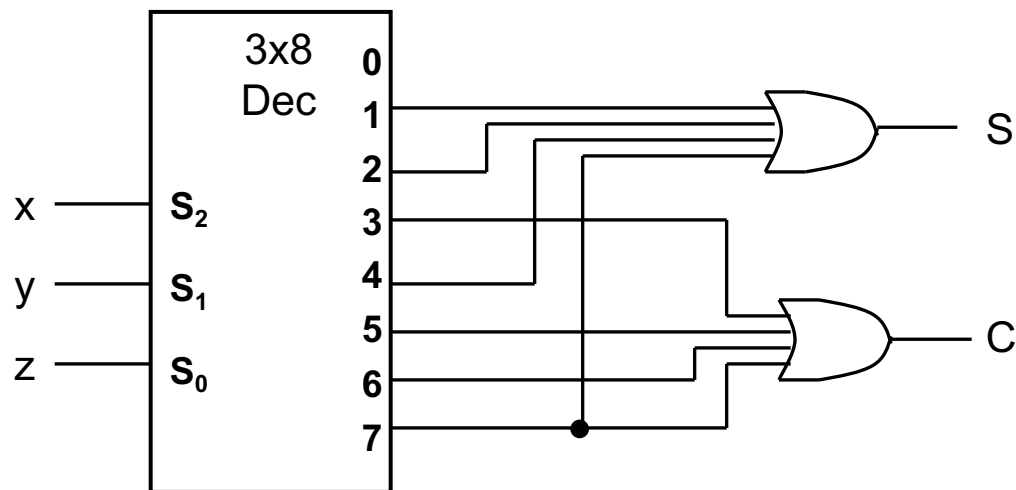

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Decoder Chip

 - 74138
 - An standard decoder
 - Active-low outputs
 - Three Enable




74138: Function Table

Inputs					Outputs							
Enable		Select										
$G1$	$\overline{G2}^*$	C	B	A	$Y0$	$Y1$	$Y2$	$Y3$	$Y4$	$Y5$	$Y6$	$Y7$
H	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	H	L	H	H	H	H
H	L	H	L	L	H	H	H	H	L	H	H	H
H	L	H	L	H	H	H	H	H	H	L	H	H
H	L	H	H	L	H	H	H	H	H	H	L	H
H	L	H	H	H	H	H	H	H	H	H	H	L
x	H	x	x	x	H	H	H	H	H	H	H	H
L	x	x	x	x	H	H	H	H	H	H	H	H

$$\overline{G2}^* = \overline{G2A} + \overline{G2B}$$

74138: Logic Circuit

 


Sample 3

- Implement function f using decoder
 - $f(A,B,C) = \prod M(2,3,5)$

Implement f Using 74X138

- Implement function f using decoder
 - $f(A,B,C) = \prod M(2,3,5)$

 


Sample 4

- Implement function f using an active low decoder
 - $f(A,B,C) = \sum m(0,1,4,6,7)$

Decoder as a logic block: Sample 7 (cont'd)

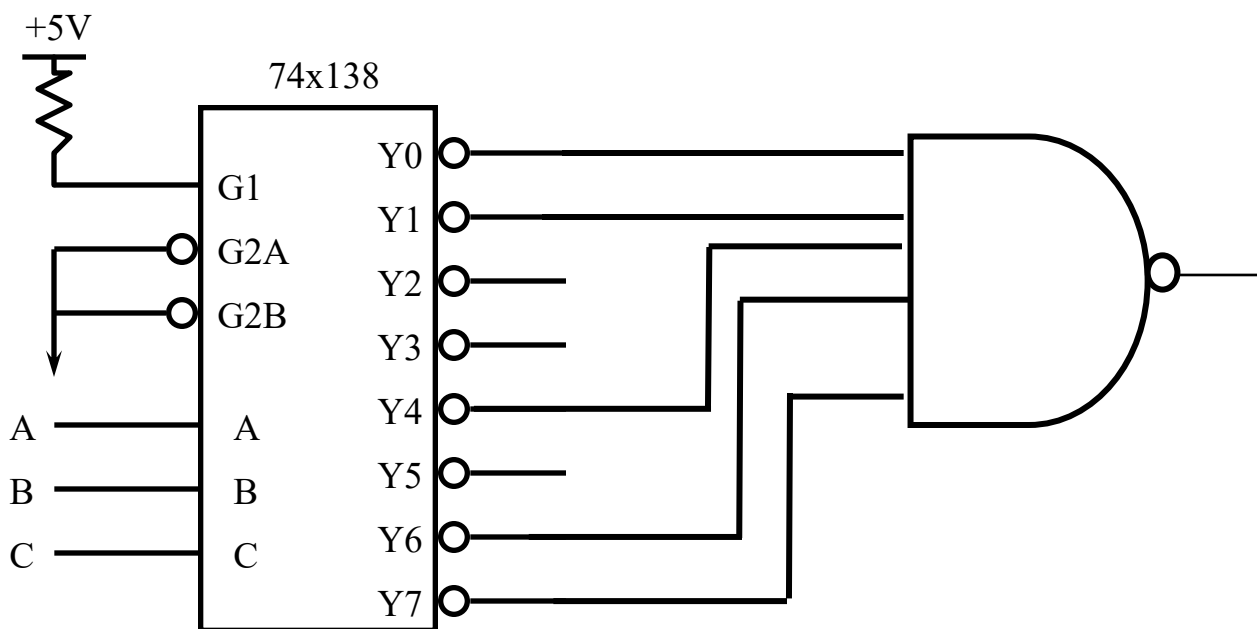
- Implement function f using an active low decoder
 - $f(A,B,C) = \sum m(0,1,4,6,7)$




7-Segment Decoder

7-Segment LED Displays

 - Display numbers
- 7 light emitting diodes (LED)
- Each LED controlled by an input
 - 1 means “on”
 - 0 mean “OFF”



Digit	Display	gfedcba	abcdefg	a	b	c	d	e	f	g
0	0	0x3F	0x7E	on	on	on	on	on	on	off
1	1	0x06	0x30	off	on	on	off	off	off	off
2	2	0x5B	0x6D	on	on	off	on	on	off	on
3	3	0x4F	0x79	on	on	on	on	off	off	on
4	4	0x66	0x33	off	on	on	off	off	on	on
5	5	0x6D	0x5B	on	off	on	on	off	on	on
6	6	0x7D	0x5F	on	off	on	on	on	on	on
7	7	0x07	0x70	on	on	on	off	off	off	off
8	8	0x7F	0x7F	on	on	on	on	on	on	on
9	9	0x6F	0x7B	on	on	on	on	off	on	on
A	A	0x77	0x77	on	on	on	off	on	on	on
b	b	0x7C	0x1F	off	off	on	on	on	on	on
C	C	0x39	0x4E	on	off	off	on	on	on	off
d	d	0x5E	0x3D	off	on	on	on	on	off	on
E	E	0x79	0x4F	on	off	off	on	on	on	on
F	F	0x71	0x47	on	off	off	off	on	on	on


 


7-Segment : Types

- Two types
 - Common- anode
 - Common-cathode



7-Segment : Common-Anode

  - Anode of all of the LEDs are tied together to power supply




7-Segment: Common-Cathode

  - Cathode of all of the LEDs are tied together to ground



7-Segment Decoder

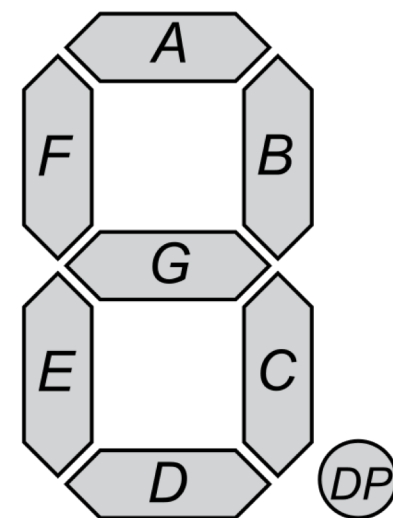- **Input**
 - 4-bit BCD code
- **Output**
 - 7-bit code
- **Function**
 - Display decimal code
- **Example**
 - Input: $(0000)_{\text{BCD}}$
 - Output: $(1111110)_{\text{7-segment}}$




Digit	Display	gfedcba	abcdefg	a	b	c	d	e	f	g
0		0x3F	0x7E	on	on	on	on	on	on	off

7-Segment Decoder: Truth Table


Digit	ABCD	abcdefg
0	0000	1111110
1	0001	0110000
2	0010	1101101
3	0011	1111001
4	0100	0110011
5	0101	1011011
6	0110	1011111
7	0111	1110000
8	1000	1111111
9	1001	1110011

Digit	ABCD	abcdefg
10	1010	XXXXXXXX
11	1011	XXXXXXXX
12	1100	XXXXXXXX
13	1101	XXXXXXXX
14	1110	XXXXXXXX
15	1111	XXXXXXXX


7-Segment Decoder: K-Map

 

a

 

b

 

c

$$\begin{aligned} a &= A + B D + C + B' D' \\ b &= A + C' D' + C D + B' \\ c &= A + B + C' + D \end{aligned}$$

7-Segment Decoder: K-Map

AB		A			
		00	01	11	10
CD	00	1	0	X	1
	01	0	1	X	0
	11	1	0	X	X
	10	1	1	X	X
		B			
		D			

d

AB		A			
		00	01	11	10
CD	00	1	0	X	1
	01	0	0	X	0
	11	0	0	X	X
	10	1	1	X	X
		B			
		D			

e

AB		A			
		00	01	11	10
CD	00	1	1	X	1
	01	0	1	X	1
	11	0	0	X	X
	10	0	1	X	X
		B			
		D			

f


$$d = B' D' + C D' + B C' D + B' C$$

$$e = B' D' + C D$$

$$f = A + C' D' + B D' + B C'$$



7-Segment Decoder: K-Map
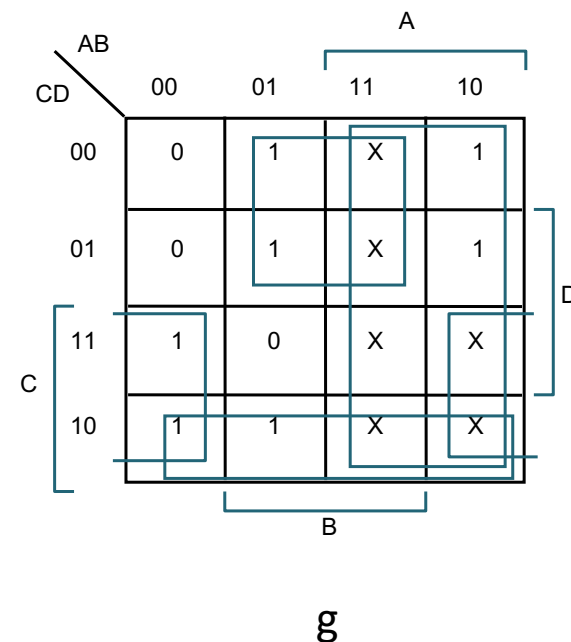
$$\begin{aligned}
 a &= A + B D + C + B' D' \\
 b &= A + C' D' + C D + B' \\
 c &= A + B + C' + D \\
 d &= B' D' + C D' + B C' D + B' C \\
 e &= B' D' + C D \\
 f &= A + C' D' + B D' + B C' \\
 g &= A + C D' + B C' + B' C
 \end{aligned}$$



BCD to 7-Segment Decoder

- 74LS47

  

Thank You

